## Science Lesson

Instructor:

Time: 45-60 Minutes

## **Making Batteries**

Lesson Goal: Students will be able to identify and understand how electricity is made. Using fruits and vegetables, students will create direct current batteries capable of powering DC powered devices.

#### Materials:

- 1. Fresh lemons and potatoes
- 2. 14 ga. or larger copper wire
- 3. 16 penny steel nail or screw, non-coated
- 4. Digital or analog multimeter to measure voltage and current
- 5. Alligator clips as leads
- 6. Any 12 VDC device: test bulb, radio, Walkman or similar device.

#### Performance Objectives:

- 1. Understand how electricity is produced.
- 2. Distinguish between Direct Current (DC) and Alternating Current (AC).
- 3. Understand what series and parallel circuitry is.
- 4. Produce a battery with enough power to make a 12VDC device run.

#### **Teaching Activities:**

- 1. Explain the fundamentals of electricity.
- 2. Set up experiment to allow students to make lemon and potato batteries.
- 3. Discuss why you need several potatoes and lemons to make the 12VDC device work.
- 4. Have fun with the experiment

#### Student Activities:

- 1. Understand electricity and its complexities.
- 2. Participate in class discussion.
- 3. Do class experiment.
- 4. Ask questions as needed.

#### Reflections on the Lesson:

# **Science Lesson**

### **Making Batteries**

### Directions:

- 1. Take a potato or a lemon.
- 2. Place a copper wire at one end of the potato or lemon and place the steel nail or screw at the other end.
- 3. Place one lead on the copper wire.
- 4. Place another lead on the nail.
- 5. Take the multimeter and set the meter to read up to 12 volts.
- 6. Place the red lead on the copper wire.
- 7. Place the black lead on the nail.
- 8. Record the volts
- 9. Hint: if the volts read negative, switch the leads.
- 10. Make enough batteries to power the 12VDC Device.

#### Questions

- 1. Who invented batteries?
- 2. What is happening between the copper wire and the nail/screw?
- 3. What happens as you connect the batteries together?
- 4. What types of circuit are you making, and why?
- 5. Which do you think is better as a battery: the potato or the lemon? Why?